

Q1- In the construction of an electrical circuit a  $5.00\mu\text{F}$  capacitor was accidentally used instead of the required  $16.0\mu\text{F}$  capacitor? What value capacitor must a technician add to correct this circuit without removing existing circuit elements? Must any connections be broken in the process?

The capacity of combination of two capacitors in parallel is the sum of the capacitance of the two individual capacitors hence adding a capacitor of  $11\mu\text{F}$  in parallel to the  $5\mu\text{F}$  capacitor results in the total capacity of  $16\mu\text{F}$ .

Without breaking any connection the new capacitor can be soldered with the previous one in parallel.

Answer:  $11\mu\text{F}$  in parallel.

Q2- The specifications on a light bulb is  $1\text{W}$ ,  $6\text{V}$ . What is the minimum resistance of a resistor that is required to be able to use it with a  $12\text{V}$  battery and how it must be connected?

The power dissipated in a circuit is given by  $P = V^2/R$

Hence the resistance of the bulb will be  $R = V^2/P = 36/1 = 36\Omega$ .

Hence a resistance of  $36\Omega$  in series will divide the potential drop of the  $12\text{V}$  batteries in two equal parts of  $6\text{V}$  and the potential difference across the bulb will be safe  $6\text{V}$ .

The resistance of  $36\Omega$  should be connected in series with the bulb.

Q3- Three identical light bulbs are connected in series across a potential difference  $V$ . This combination dissipates  $5.0\text{W}$  energy. What is the total amount of energy dissipated if the bulbs are connected in parallel with the same potential difference?

Let the resistance of each bulb is  $R$  then the resistance of the combination will be  $3R$ .

The power dissipated in the circuit will be

$$P = V^2/(3R) = 5.0\text{W}$$

Gives  $V^2 = 15.0 R$  ----- (1)

Now if the bulbs are connected in parallel then the equivalent resistance will be

$R' = R/3$  and hence the power will be given by

$$P' = V^2/(R/3) = 3V^2/R$$

Substituting value of  $V^2/(3R)$  from equation 1 we get

$$P' = V^2/(R/3) = 3 \cdot 5.0\text{W} = 15.0\text{W}$$