

Q- A  $2.8\text{k}\Omega$  and a  $2.1\text{k}\Omega$  resistor are connected in parallel; this combination is connected in series to a  $1.8\text{k}\Omega$  resistor. If each resistor is rated at  $0.50\text{W}$ , what is the maximum voltage that can be applied across the whole network without damaging resistors?

Power dissipated in a resistor is given by  $P = I^2R$  hence maximum current allowed in the three resistors is given by

$$I_1 = \sqrt{\frac{P}{R_1}} = \frac{0.5}{2.8 \times 10^3} = 13.4 \text{ mA}$$

$$I_2 = \sqrt{\frac{P}{R_2}} = \frac{0.5}{2.1 \times 10^3} = 15.4 \text{ mA}$$


And  $I = \sqrt{\frac{P}{R_3}} = \frac{0.5}{1.8 \times 10^3} = 16.7 \text{ mA}$

As the current in  $1.8\text{K}$  resistor is divided in the other two and will be less, the maximum current allowed in the circuit is  $16.7 \text{ mA}$ .

As the two resistors are in parallel, the voltage across them is same and thus

$$I_1 R_1 = I_2 R_2$$

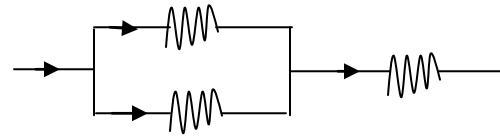Or  $\frac{I_1}{I_2} = \frac{R_2}{R_1} = \frac{2.1}{2.8} = \frac{3}{4}$



Hence current in  $2.8\text{K}$  will be  $I_1 = (3/7) \times 16.7 = 7.16 \text{ mA}$

And in  $2.1 \text{ K}$  will be  $I_2 = (4/7) \times 16.66 = 9.52 \text{ mA}$

Thus the maximum voltage will be

$$V = 7.16 \times 10^{-3} \times 2.8 \times 10^3 + 16.7 \times 10^{-3} \times 1.8 \times 10^3 = 50.1 \text{ V.}$$