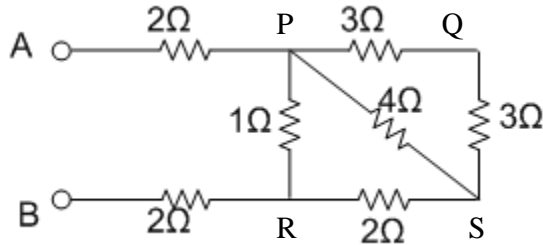


(a) Consider the circuit below.



a) Find the equivalent resistance of the combination.

As the two  $3\Omega$  resistances are in series their equivalent resistance will be  $6\Omega$  and this is connected in parallel to  $4\Omega$  this gives the resistance between points P and S equal to

$$R_{PS} = \frac{6 * 4}{6 + 4} = 2.4\Omega$$

This  $2.4\Omega$  resistance is in series with  $2\Omega$  resistance (SR) gives a total of  $4.4\Omega$

This resistance is in series with  $1\Omega$  resistance in parallel and hence the equivalent resistance between points P and R will be given by

$$R_{PR} = \frac{1 * 4.4}{1 + 4.4} = 0.8\Omega$$

The circuit reduces to three resistances in series and thus the equivalent resistance of the circuit will be

$$R_{AB} = 2 + 0.8 + 2 = 4.8\Omega$$

b) If a 10V potential difference (PD) is applied across the points A and B, find the PD across the  $4\Omega$  resistor and current in it.

The current in the circuit when a 10V voltage is applied to AB will be

$$I = V/R = 10/4.8 = 2.08 \text{ A}$$

Hence the Potential difference across  $0.8\Omega$  resistor or between points P and R is given by

$$V_{PR} = 2.08 * 0.8 = 1.66 \text{ V.}$$

Hence the current in PSR branch in will be

$$I_1 = 1.66/4.4 = 0.38 \text{ A}$$

Thus the potential different between points P and S will be

$$V_{PS} = 0.38 * 2.4 = 0.9 \text{ V}$$

And the current in the  $4\Omega$  resistance will be

$$I_2 = 0.9/4 = 0.23 \text{ A}$$