

Q- A 2.00-nF capacitor with an initial charge of  $5.10 \mu\text{C}$  is discharged through a  $1.30\text{-k}\Omega$  resistor.

(a) Calculate the current in the resistor  $9.00 \mu\text{s}$  after the resistor is connected across the terminals of the capacitor.

The time constant of the capacitor resistor circuit is given by

$$\tau = RC = 1.30 \times 10^3 \times 2.00 \times 10^{-9} \text{ s} = 2.6 \times 10^{-6} \text{ s} = 2.6 \mu\text{s}.$$

The discharge current in the circuit as a function of time is given by

$$i = \frac{q_0}{RC} * e^{-\frac{t}{\tau}}$$

Hence the current at the given time will be

$$i = \frac{5.10 \mu\text{C}}{2.6 \mu\text{s}} * e^{-\frac{9.00 \mu\text{s}}{2.6 \mu\text{s}}} = 1.96 * 0.031 = 0.06 \text{ A}$$

(b) What charge remains on the capacitor after  $8.00 \mu\text{s}$ ?

The time constant of the capacitor resistor circuit is given by

$$\tau = RC = 1.30 \times 10^3 \times 2.00 \times 10^{-9} \text{ s} = 2.6 \times 10^{-6} \text{ s} = 2.6 \mu\text{s}.$$

The charge on the capacitor discharging through a resistance as a function of time is given by

$$q = q_0 * e^{-\frac{t}{\tau}}$$

Hence the charge on the capacitor after  $8.00 \mu\text{s}$  time

$$q = 5.10 \mu\text{C} * e^{-\frac{8.00 \mu\text{s}}{2.6 \mu\text{s}}} = 5.10 \mu\text{C} * 0.046 = 0.235 \mu\text{C}$$

(c) What is the maximum current in the resistor?

The current in the circuit is the maximum at  $t = 0$  hence the maximum current will be

$$i = \frac{q_0}{RC} * e^{-\frac{0}{\tau}} = \frac{q_0}{RC} = \frac{5.10 \mu\text{C}}{2.6 \mu\text{s}} = 1.96 \text{ A}$$