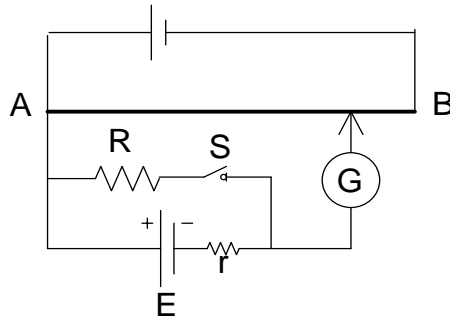


Q- The circuit below shows a circuit designed to measure the internal resistance 'r' of a battery. Resistor R is 2Ω and AB is the potentiometer wire. With the switch S open a balancing length  $l_1 = 55.2\text{cm}$ . is obtained. When switch S is closed the balancing length  $l_2 = 53.2\text{cm}$ . Calculate the internal resistance 'r' of the battery.



Let the potential gradient (rate of potential drop per unit length  $dV/dl$ ) across the wire AB is  $\rho$  Volt/cm.

When the switch S is open the length of the potentiometer wire balances the EMF of the cell (as no current through the cell the cell is in open circuit) and hence we have

$$E = \rho * l_1 = 55.2 \rho \quad \text{----- (1)}$$

When the switch S is closed there will be a current through the cell and the resistor R and hence the cell is in closed circuit and hence the terminal voltage V is balanced by the potentiometer wire length  $l_2$  and hence we have

$$V = \rho * l_2 = 53.2 \rho \quad \text{----- (2)}$$

Dividing the two equations we have

$$E/V = 55.2/53.2 = 1.0376$$

Now as the internal resistance is given by the relation

$$r = R \left( \frac{E}{V} - 1 \right)$$

Substituting the values we get

$$r = 2 \left( \frac{55.2}{53.2} - 1 \right) = 0.0752 \Omega$$