

Q- A sinusoidal voltage $v(t) = (40.0 \text{ V}) \sin(100t)$ is applied to a series RLC circuit with $L = 160 \text{ mH}$, $C = 0.9 \mu\text{F}$, and $R = 68 \text{ Ohm}$

a) What is the impedance of the circuit?

As indicated by the equation $V_{\max} = 40.0 \text{ V}$ and $\omega = 100 \text{ radians/sec}$.

Hence the inductive reactance of the circuit will be

$$X_L = L\omega = 160 * 10^{-3} * 100 = 16 \Omega$$

And the capacitive reactance will be

$$X_C = 1/(C\omega) = 1/(0.9 * 10^{-6} * 100) = 1.11 * 10^4 \Omega$$

Now the impedance of the circuit is given by

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Or
$$Z = \sqrt{68^2 + (16 - 1.11 * 10^4)^2} = 11084.21 \Omega$$

(b) What is the maximum current?

The peak value of voltage (maximum) is 40V and hence maximum current in the circuit is given by

$$\begin{aligned} I_{\max} &= V_{\max}/Z \\ &= 40.0/11084.21 = 3.61 * 10^{-3} \text{ A} \end{aligned}$$

(c) Determine Phase angle in the equation $i(t) = I_{\max} \sin(\omega t - \text{Phase angle})$ and the average power in the circuit.

The maximum current is already calculated and equal to 3.61 mA

The phase angle is given by

$$\tan \phi = \frac{(X_L - X_C)}{R} = \frac{-11084}{68} = -163$$

Gives $\phi = -89.65^\circ$

The average power in the LCR circuit is given by

$$\langle P \rangle = \frac{i_{\max}^2 R}{2} = \frac{(3.61 * 10^{-3})^2 * 68}{2} = 4.43 * 10^{-4} \text{ W}$$