

Q- Two resistors connected in series have an equivalent resistance of $690\ \Omega$. When they are connected in parallel, their equivalent resistance is $150\ \Omega$. Find the resistance of each resistor.

Let the resistances are R_1 and R_2 .

When the resistances are connected in series, their equivalent resistance is equal to the sum of the individual resistances and hence

$$R_s = R_1 + R_2 = 690\ \Omega. \quad \text{----- (1)}$$

When the resistances are connected in parallel, inverse of their equivalent resistance is equal to the sum of inverse of their individual resistances and hence

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{150}$$

Or $\frac{R_1 R_2}{R_1 + R_2} = 150 \quad \text{----- (2)}$

Substituting from equation 1 we have

$$R_1 R_2 = 150 * 690 = 103500$$

Substituting value of R_2 from equation 1 again we have

$$R_1 (690 - R_1) = 103500$$

$$\text{Gives } R_1^2 - 690R_1 + 103500 = 0$$

$$\text{Or } R_1 = \frac{690 \pm \sqrt{690^2 - 4 * 1 * 103500}}{2} = 469.6\ \Omega \text{ or } 220.4\ \Omega$$

Hence R_1 and R_2 are **469.6Ω and 220.4Ω** respectively.