

Q- A series combination of $R = 1000\Omega$, $L = 500 \text{ mH}$ and $C = 150\mu\text{F}$ is connected to a sinusoidal voltage supply of frequency 50Hz . The circuit has peak amplitude of 1A . Calculate the voltage amplitude of the supply generator.


The current in an AC circuit is opposed by resistance and reactance both.

The voltage is ahead of current by a phase difference of 90° and in inductor and lagging behind by 90° in a capacitor. Hence the total reactance in the circuit is considered as the difference of the two reactance and is given by

$$X = X_L - X_C = 2\pi fL - \frac{1}{2\pi fC}$$

Now as the total voltage across the resistance and the reactance is having a phase difference equal to 90° , the resultant oppose of the circuit is called impedance Z of the circuit and is given by
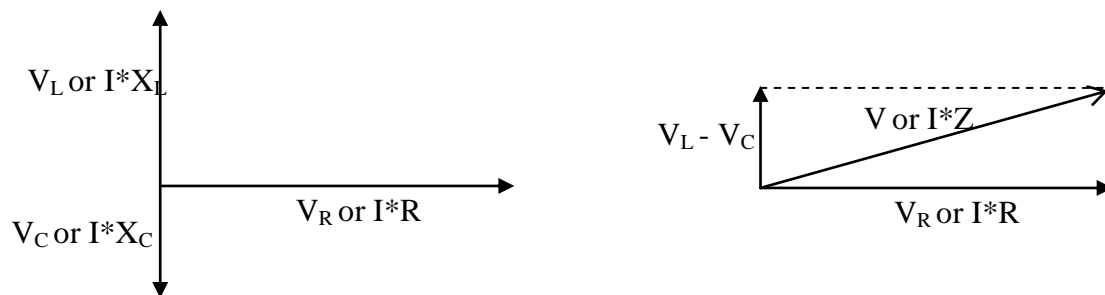
$$Z = \sqrt{R^2 + X^2} = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{R^2 + \left(2\pi fL - \frac{1}{2\pi fC}\right)^2}$$



Hence the voltage amplitude across the whole circuit or of the supply generator is given by

$$V = I * Z$$

$$\text{Or } V = I * Z = I * \sqrt{R^2 + \left(2\pi fL - \frac{1}{2\pi fC}\right)^2}$$

$$\text{Or } V = 1 * \sqrt{1000^2 + \left(2\pi * 50 * 500 * 10^{-3} - \frac{1}{2\pi * 50 * 150 * 10^{-6}}\right)^2}$$

$$\text{Or } V = \sqrt{1000^2 + (157.1 - 21.2)^2} = \sqrt{1000^2 + 135.9^2} = 1009.2 \text{ V}$$