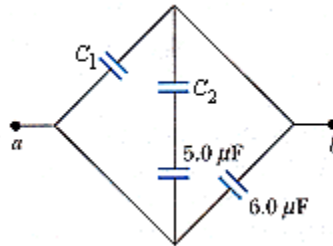


Q- Find the equivalent capacitance between points  $a$  and  $b$  in the combination of capacitors shown in Figure.  $C_1 = 2.0 \mu\text{F}$  and  $C_2 = 3.0 \mu\text{F}$ .



Looking minutely both terminals of  $C_1$  and  $6.0 \mu\text{F}$  capacitors are connected directly between the  $a$  and  $b$ . Similarly the series connection of  $5.0 \mu\text{F}$  and  $C_2$  is also connected directly to  $a$  and  $b$ . Thus the circuit is having  $C_1$ ,  $6.0 \mu\text{F}$  capacitors and the series combination of  $5.0 \mu\text{F}$  and  $C_2$  are in parallel as in figure. The equivalent capacitance of the series combination of  $5.0 \mu\text{F}$  and  $C_2$  is equal to (units are in  $\mu\text{F}$ )

$$\frac{C_2 * 5.0}{C_2 + 5.0}$$

Thus the equivalent capacitance of the circuit is given by

$$C = C_1 + 6.0 + \frac{C_2 * 5.0}{C_2 + 5.0}$$

Or  $C = 2.0 + 6.0 + \frac{3.0 * 5.0}{3.0 + 5.0} = 9.875 \mu\text{F}$

