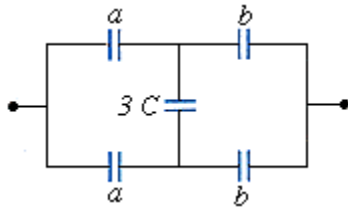


Q- Determine the equivalent capacitance of the combination shown in Figure, where $a = 10C$ and $b = 45C$.



As the upper and lower branches are symmetric and parallel, the potential difference across the capacitor $3C$ will be zero and the capacitor will not get any charge. Thus the circuit can be considered as the parallel combinations of two branches with a and b in series.

The equivalent capacitance of a and b in series will be

$$\frac{ab}{a+b} = \frac{10C \cdot 45C}{10C + 45C} = \frac{90C}{11}$$

As the equivalent circuit is the parallel combination of the two series, its capacitance is given by

$$C_{\text{equivalent}} = 2 * \frac{90C}{11} = \frac{180C}{11} = 16.4 C$$