

Q- Two capacitors $C_1 = 30 \mu\text{F}$ and $C_2 = 60 \mu\text{F}$ are connected in series with a 12 V battery. Find

(a) The charge on C_1 and

(b) The potential difference across C_2 .

When two or more than two capacitors are connected in series the voltage across the combination is distributed between them. The equivalent capacitance is given by

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

Or
$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2} = \frac{30 \times 10^{-6} \times 60 \times 10^{-6}}{30 \times 10^{-6} + 60 \times 10^{-6}} = 20 \times 10^{-6} \text{ F}$$

(a) The charge on the combination is given by

$$Q = CV = 20 \times 10^{-6} \times 12 = 2.4 \times 10^{-4} \text{ C}$$

In series combination of capacitors charge on each capacitor will be same which is equal to the charge from battery thus the charge on capacitor C_1 will also be **$2.4 \times 10^{-4} \text{ C}$** .

(b) The charge on C_2 is also $2.4 \times 10^{-4} \text{ C}$, thus the potential difference across C_2 is given by

$$V_2 = Q_2 / C_2 = 2.4 \times 10^{-4} / 60 \times 10^{-6} = \mathbf{4.0 \text{ V}}$$