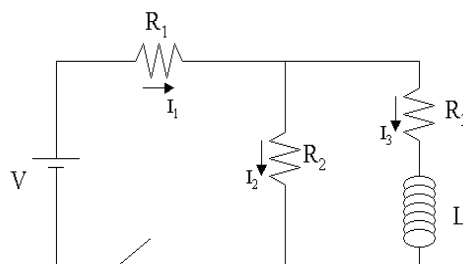


Q- Three resistors ( $R_1 = 120 \text{ Ohms}$ ,  $R_2 = 330 \text{ Ohms}$ , and  $R_3 = 240 \text{ Ohms}$ ) and an ideal inductor ( $L = 1.6 \text{ mH}$ ) are connected to a battery ( $V = 9 \text{ V}$ ) through a switch as shown in the figure. The switch has been open for a long time before it is closed at  $t = 0$ . At what time  $t$ , does the current through the inductor ( $I_3$ ) reach a value that is 63% of its maximum value?

Here as soon as the switch is closed the current starts flowing in the  $R_1 R_2$  loop due to which there will be a potential difference across  $R_2$  which force a current in the series of  $R_3$  and the inductor  $L$ . Due to electromagnetic induction an EMF will be induced in the inductor which changes with time and hence the currents in both loop changes. Let at time  $t$  after the switch is closed, the currents in the three parts are  $I_1$ ,  $I_2$  and  $I_3$  respectively.



According to junction law the charge will not accumulate at any junction we have

$$I_1 = I_2 + I_3 \quad \text{----- (1)}$$

As  $R_2$  is in parallel with  $R_3$  and  $L$  the potential difference across the two branches will be equal and this gives

$$I_2 R_2 = I_3 R_3 + L \cdot (dI_3/dt) \quad \text{----- (2)}$$

As the EMF of the battery is dropped in the left loop, using loop rule we get

$$\varepsilon = I_1 R_1 + I_2 R_2 \quad \text{----- (3)}$$

Substituting the value of  $I_1$  from equation 1 in 3 we get

$$\varepsilon = (I_2 + I_3) R_1 + I_2 R_2 = I_2 (R_1 + R_2) + I_3 R_1$$

Or 
$$I_2 = \frac{\varepsilon - I_3 R_1}{(R_1 + R_2)} \quad \text{----- (4)}$$

Substituting this value of  $I_2$  in equation 2 we get

$$\frac{\varepsilon - I_3 R_1}{(R_1 + R_2)} * R_2 = I_3 R_3 + L \frac{dI_3}{dt}$$

$$\text{Or } L \frac{dI_3}{dt} = \frac{\varepsilon - I_3 R_1}{(R_1 + R_2)} * R_2 - I_3 R_3$$

$$\text{Or } L \frac{dI_3}{dt} = \frac{\varepsilon R_2 - I_3 (R_1 R_2 + R_1 R_3 + R_2 R_3)}{(R_1 + R_2)}$$

$$\text{Or } \frac{dI_3}{\varepsilon R_2 - I_3 (R_1 R_2 + R_1 R_3 + R_2 R_3)} = \frac{dt}{L(R_1 + R_2)}$$

Integrating with proper limits we have (initially current in the inductance is zero)

$$\int_0^{I_3} \frac{dI_3}{\varepsilon R_2 - I_3 (R_1 R_2 + R_1 R_3 + R_2 R_3)} = \int_0^t \frac{dt}{L(R_1 + R_2)}$$

$$\text{Or } -\frac{1}{(R_1 R_2 + R_1 R_3 + R_2 R_3)} \ln \left[ \frac{\varepsilon R_2 - I_3 (R_1 R_2 + R_1 R_3 + R_2 R_3)}{\varepsilon R_2} \right] = \frac{t}{L(R_1 + R_2)}$$

$$\text{Or } \ln \left[ \frac{\varepsilon R_2 - I_3 (R_1 R_2 + R_1 R_3 + R_2 R_3)}{\varepsilon R_2} \right] = -\frac{(R_1 R_2 + R_1 R_3 + R_2 R_3)t}{L(R_1 + R_2)}$$

$$\text{Or } \left[ 1 - \frac{I_3 (R_1 R_2 + R_1 R_3 + R_2 R_3)}{\varepsilon R_2} \right] = e^{-\frac{(R_1 R_2 + R_1 R_3 + R_2 R_3)t}{L(R_1 + R_2)}}$$

$$\text{Or } I_3 = \frac{\varepsilon R_2}{(R_1 R_2 + R_1 R_3 + R_2 R_3)} \left[ 1 - e^{-\frac{(R_1 R_2 + R_1 R_3 + R_2 R_3)t}{L(R_1 + R_2)}} \right]$$

The elements in the circuit shown above have the following values:  $\varepsilon = 9 \text{ V}$ ,  $L = 1.6 \text{ mH}$ ,  $R_1 = 120 \text{ } \Omega$ ,  $R_2 = 330 \text{ } \Omega$  and  $R_3 = 240 \text{ } \Omega$ .

$$I_3 = \frac{9*330}{120*330+120*240+330*240} [1 - e^{-(120*330+120*240+330*240)t}]$$

$$\text{Or } I_3 = 0.021[1 - e^{-147600*t}]$$

The current is maximum at long time and will be 0.021 A. hence the required time t is given by

$$0.021 * \frac{63}{100} = 0.021[1 - e^{-147600*t}]$$

Or  $\frac{63}{100} = 1 - e^{-147600*t}$

Or  $e^{-147600*t} = 1 - \frac{63}{100}$

Or  $e^{-147600*t} = 0.37$

Or  $e^{147600*t} = 2.703$

Or  $147600 * t = \ln 2.703$

Or  $147600 * t = 0.994$

Or  $t = 6.74*10^{-6} \text{ s}$

www.physicshelpline.com