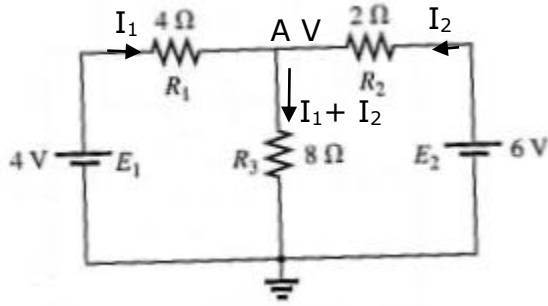


Q- Find current through all resistances in the given network.



Let the current in the loops are I_1 and I_2 as in the figure and the potential at node A be V .

Using Ohms law, we can write the equations for the current in the three resistors we get (the potential of the grounded portion is zero)

$$E_1 - V = I_1 R_1$$

Or $4 - V = I_1 * 4$

Or $I_1 = (4-V)/4$ ----- (1)

$$E_2 - V = I_2 R_2$$

Or $6 - V = I_2 * 2$

Or $I_2 = (6-V)/2$ ----- (2)

And

$$V - 0 = (I_1 + I_2) R_3$$

Or $V = 8 I_1 + 8 I_2$ ----- (3)

Substituting the values of currents from equations 1 and 2 in equation 3 we get

$$V = 8 * \left[\frac{4-V}{4} + \frac{6-V}{2} \right]$$

Gives $V = 8 - 2V + 24 - 4V$

Or $V = 32/7$ volt

Substituting in equation 1 we get

$$I_1 = 1 - (8/7) = - 1/7 \text{ A} = - 0.143 \text{ A}$$

And from equation 2 we get

$$I_2 = 3 - (16/7) = 5/7 \text{ A} = 0.714 \text{ A}$$

And hence

$$I_3 = I_1 + I_2 = -(1/7) + (5/7) = 4/7 \text{ A} = 0.571 \text{ A}$$