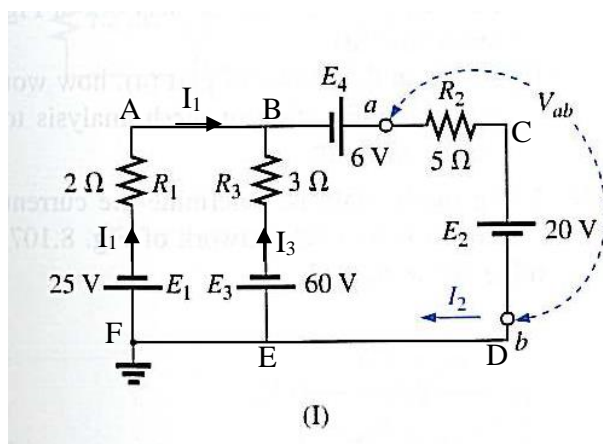


Q- Find the mesh currents and voltage  $V_{ab}$  for given network.



Let the currents in the different branches are as indicated in figure.

Considering the junction law for nod B we get

$$I_1 - I_2 + I_3 = 0$$

$$\text{Or } I_3 = I_2 - I_1 \quad \text{----- (1)}$$

Considering mesh ABEFA (clockwise positive) we have

$$\Sigma E = E_3 - E_1$$

$$\text{And } \Sigma IR = I_1 R_1 - I_3 R_3$$

Applying Kirchhoff's law we have

$$\Sigma E = \Sigma IR$$

$$\text{Or } E_3 - E_1 = I_1 R_1 - I_3 R_3$$

$$\text{Or } 60 - 25 = 2 I_1 - 3 I_3$$

$$\text{Or } 2 I_1 - 3 I_3 = 35 \quad \text{----- (2)}$$

Considering mesh BCDEB (clockwise positive) we have

$$\Sigma E = E_4 - E_2 - E_3$$

$$\text{And } \Sigma IR = I_2 R_2 + I_3 R_3$$

Applying Kirchhoff's law we have

$$\Sigma E = \Sigma IR$$

$$\text{Or } E_4 - E_2 - E_3 = I_2 R_2 + I_3 R_3$$

$$\text{Or } 6 - 20 - 60 = 5 I_2 + 3 I_3$$

$$\text{Or } 5 I_2 + 3 I_3 = -74 \quad \text{----- (3)}$$

Substituting values of  $I_3$  in equations 2 and 3 in equation 1 we get

$$2 I_1 - 3 (I_2 - I_1) = 35$$

$$\text{Or } 5 I_1 - 3 I_2 = 35 \quad \text{----- (2A)}$$

$$\text{And } 5 I_2 + 3 (I_2 - I_1) = -74$$

$$\text{Or } -3 I_1 + 8 I_2 = -74 \quad \text{----- (3A)}$$

Equation  $(2A)*3 + (3A)*5$  gives

$$31 I_2 = - 265$$

Or  $I_2 = - 265/31 = - 8.55 \text{ A}$

Using equation (2A) we have

$$5I_1 - 3(- 8.55) = 35$$

Gives  **$I_1 = 1.87 \text{ A}$**

And  **$I_3 = I_2 - I_1 = - 8.55 - 1.87 = - 10.42 \text{ A}$**

Now  $V_{ab} = V_a - V_b =$  potential drop across  $R_2$  and across  $E_2$

Or  $V_{ab} = I_2 R_2 - E_2 = - 8.55*5 - (-20) = - 22.75 \text{ V}$