

Q- A source of alternating voltage $e = 10\sqrt{2} \sin \omega t$ is connected to a resistor $R = 100 \Omega$ and a capacitor $C = 0.5 \mu\text{F}$ in series.

(a) Plot impedance Z_T and phase difference between current and voltage θ_T versus frequency for a frequency range of zero to 10 kHz.

(b) Plot voltage across capacitor V_C versus frequency for the frequency range of part (a)

(c) Plot voltage across resistor V_R versus frequency for the frequency range of part (a).

The source voltage across the circuit is

$$V = 10 \sqrt{2} \sin \omega t$$

Resistance $R = 100 \Omega$

Capacitance $C = 0.5 \mu\text{F}$ and

Angular frequency $\omega = 2\pi n$


(a) Plot Z_T and θ_T versus frequency for a frequency range of zero to 10 kHz.

The impedance of the circuit is given by

$$Z = \sqrt{R^2 + X_C^2} = \sqrt{100^2 + \left(\frac{1}{C\omega}\right)^2} = \sqrt{100^2 + \left(\frac{1}{0.5 \times 10^{-6} \times 2 \times 3.14 \times n}\right)^2}$$

$$\text{Or } Z = \sqrt{100^2 + \left(\frac{1.01}{n^2}\right)} = \sqrt{10^4 + \left(\frac{1.01 \times 10^{11}}{n^2}\right)}$$

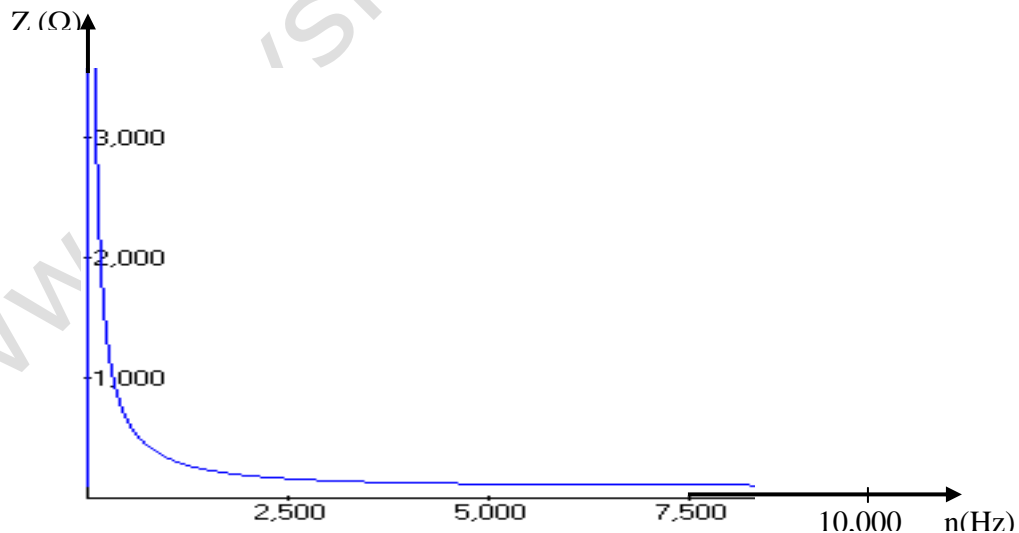For $n = 0$, $Z = \infty$; for $n = 10 \text{ k Hz}$, $Z = 104.95 \Omega$. The Z - n plot will be given as bellow




The phase difference θ between the voltage and current will depend on the frequency and is given by

$$\theta = \tan^{-1} \left(\frac{X_L - X_C}{R} \right) = \tan^{-1} \left(\frac{-1}{R \cdot C \omega} \right)$$


$$\text{Or } \theta = \tan^{-1} \left(\frac{-1}{100 \times 0.5 \times 10^{-6} \times 2 \times 3.14 \times n} \right)$$
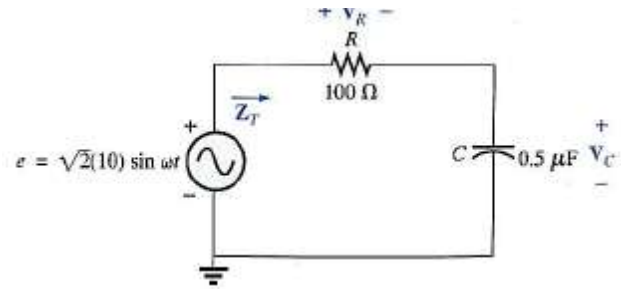
$$\text{Or } \theta = \tan^{-1} \left(-\frac{3184.7}{n} \right)$$



For $n = 0$, $\theta = -90^\circ$ and for $n = 10000$, $\theta = -17.67^\circ$

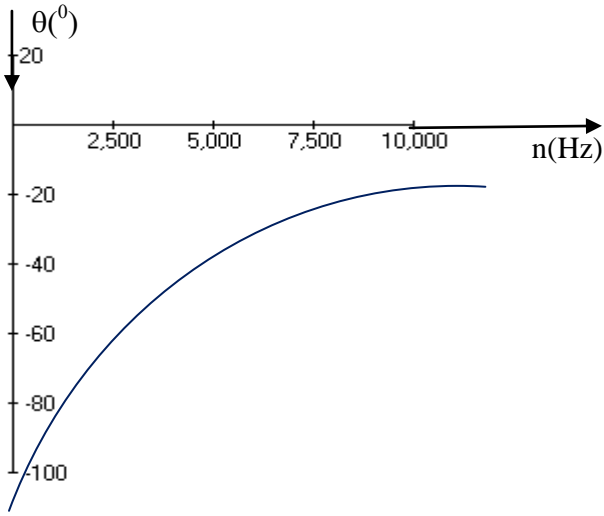The qualitative plot is shown in the figure given below



(b) Plot V_C versus frequency for the frequency range of part (a).

The source voltage across the circuit is

$$V = 10 \sqrt{2} \sin \omega t$$

Thus the effective voltage across the circuit is given by

$$V_{eff} = V_{rms} = \frac{10\sqrt{2}}{\sqrt{2}} = 10 \text{ V}$$

Hence the current in the circuit is given by

$$I_{eff} = \frac{V_{eff}}{Z} = \frac{10}{\sqrt{100^2 + \left(\frac{1}{C\omega}\right)^2}}$$

And hence the voltage across the capacitor is given by


$$V_C = I_{eff} * X_C = \frac{10}{\sqrt{100^2 + \left(\frac{1}{C\omega}\right)^2}} * \frac{1}{C\omega}$$

$$\text{Or } V_C = \frac{10}{\sqrt{10^4 * (C\omega)^2 + 1}} = \frac{10}{\sqrt{10^4 * (C * 2\pi n)^2 + 1}} = \frac{10}{\sqrt{10^{-7} * n^2 + 1}}$$

$$\text{Or } V_C = \frac{10}{\sqrt{10^{-7} * n^2 + 1}} \quad (\pi^2 \approx 10)$$

For $n = 0$, $V_C = 10 \text{ V}$ and for $n = 10000$, $V_C = 3.015 \text{ V}$

The plot is shown in figure.

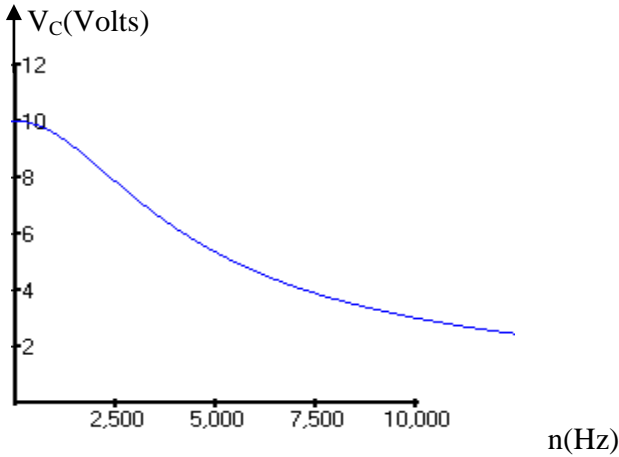

(c) Plot V_R versus frequency for the frequency range of part (a).

As above in part b, the current in the circuit is given by

$$I_{eff} = \frac{V_{eff}}{Z} = \frac{10}{\sqrt{100^2 + \left(\frac{1}{C\omega}\right)^2}}$$

The voltage across the resistor R is given by

$$V_R = I_{eff} * R = \frac{10R}{\sqrt{100^2 + \left(\frac{1}{C\omega}\right)^2}}$$

$$\text{Or } V_R = \frac{10 * 100}{\sqrt{10^4 + \left(\frac{1}{C\omega}\right)^2}} = \frac{1000}{\sqrt{10^4 + \left(\frac{1}{C * 2\pi n}\right)^2}} = \frac{10}{\sqrt{1 + \frac{10^7}{n^2}}}$$

$$\text{Or } V_R = \frac{10}{\sqrt{1 + \frac{10^7}{n^2}}} \quad (\pi^2 \approx 10)$$

For $n = 0$, $V_R = 0$ and for $n = 10000$, $V_R = 9.53$ V

The plot is shown in the figure bellow

