

Q- For the network of Figure,

- determine the value of R for maximum power to R.
- Determine the maximum power to R.

Let the current through the resistance  $R_1$  is  $I_1$ ,  $R_2$  is  $I_2$  and R is I.

Potential of point A (equal to potential at B and C as well) will be equal to the rise in the potential due to the battery and drop of potential through  $R_1$ , hence given by

$$V_A = E - I_1 R_1 = 24 - 4 I_1 \quad \text{----- (1)}$$

Similarly, the potential at B and C are given by using Ohm's law as

$$V_B = V_A = I_2 R_2 = 4 I_2 \quad \text{----- (2)}$$

And

$$V_C = V_A = IR \quad \text{----- (3)}$$

Applying junction rule to junction B we get

$$I_1 + 5 - I_2 - I = 0 \quad \text{----- (4)}$$

From equations 1 and 3 we get

$$I_1 = (24 - IR)/4$$

And from equation 2 and 3 we have

$$I_2 = IR/4$$

Substituting these values in equation (4) we get

$$6 - IR/4 + 5 - IR/4 - I = 0$$

Gives  $I(1 + R/2) = 11$

Or  $I = 22 / (2+R)$

Hence the power dissipated in R is given by

$$P = I^2 R = \left( \frac{22}{2+R} \right)^2 * R = 484 * \frac{R}{(2+R)^2} \quad \text{----- (A)}$$

This power is a function of R and for it to be maximum or minimum

$$\frac{dP}{dR} = 0$$

$$\text{Or } \frac{(2+R)^2 * 1 - R * 2(2+R)}{(2+R)^4} = 0$$

$$\text{Or } (2 + R)(2 + R - 2R) = 0$$

$$\text{Or } R = 2\Omega \quad (\text{negative value of R is not possible})$$

(b) When resistance R is  $2\Omega$ , the power in it is given by equation A as

$$P = 484 * \frac{2}{(2 + 2)^2} = 60.5 \text{ W}$$

