

Q- Using mesh analysis, determine the current through $R_3 = 5 \Omega$ resistance and the potential V_a .

Let the current in R_1 is I_1 , R_2 is I_2 and R_3 is I_3 . The currents other resistors are indicated in the figure using the junction law.

Using the loop law for mesh dbcd we get

$$\Sigma E = \Sigma IR$$

$$\text{Or } E_1 = I_1 R_1 + (I_1 - I_3) R_4$$

$$\text{Or } 12 = 4 I_1 + 6(I_1 - I_3)$$

$$\text{Or } 10 I_1 - 6 I_3 = 12$$

$$\text{Or } 5 I_1 - 3 I_3 = 6 \quad \text{----- (1)}$$

Using the loop law for mesh dbad we get

$$\Sigma E = \Sigma IR$$

$$\text{Or } E_1 = I_1 R_1 + I_3 R_3 + (I_3 - I_2) R_5$$

$$\text{Or } 12 = 4 I_1 + 5 I_3 + 3(I_3 - I_2)$$

$$\text{Or } 4 I_1 - 3 I_2 + 8 I_3 = 12 \quad \text{----- (2)}$$

And for mesh acda we have

$$\Sigma E = \Sigma IR$$

$$\text{Or } E_2 = I_2 R_2 - (I_3 - I_2) R_5$$

$$\text{Or } 16 = 2 I_2 - 3(I_3 - I_2)$$

$$\text{Or } 5 I_2 - 3 I_3 = 16 \quad \text{----- (3)}$$

Substituting I_1 from (1) and I_3 from (3) in equation (2) we get

$$4 \left(\frac{6+3I_3}{5} \right) - 3I_2 + 8 \left(\frac{5I_2-16}{3} \right) = 12$$

$$\text{Or } 72 + 36 I_3 - 45 I_2 + 200 I_2 - 640 = 180$$

$$\text{Or } 155 I_2 + 36 I_3 = 748 \quad \text{----- (4)}$$

Solving equations (4) + (3)*12 we get

$$215 I_2 = 940$$


$$\text{Or } I_2 = 940/215 = \mathbf{4.372 \text{ A}}$$

Substituting in equation (3) we get

$$I_3 = (5*4.372 - 16)/3 = \mathbf{1.953 \text{ A}}$$

Hence potential at b, V_a is given by
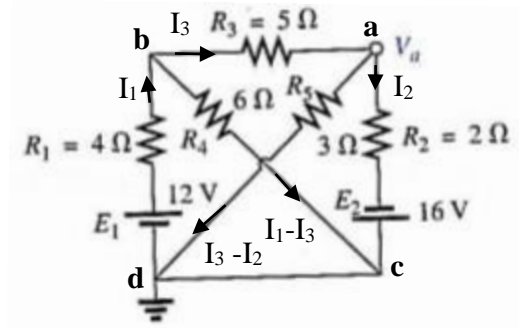
$$V_a = I_2 R_2 - E_2 = 4.372*2 - 16 = \mathbf{- 7.356 \text{ V}}$$



in