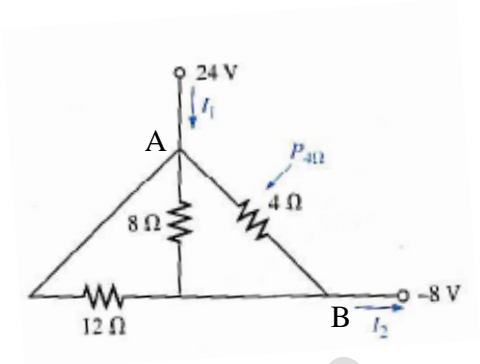


Q- For the network shown in Figure

- Find the current I_1
- Calculate the power dissipated by the $4\ \Omega$ resistor
- Find the current I_2



One end of each of the three resistors are connected to the point A and the other end of each of it is connected directly to point B. Hence all the three resistors are in parallel and connected between points A and B with potential difference $24 - (-8) = 32$ volts.

The equivalent resistance of the parallel combination of the three resistors is given by

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Or
$$\frac{1}{R} = \frac{1}{12} + \frac{1}{8} + \frac{1}{4}$$

Gives $R = 24/11 = 2.18\ \Omega$

And hence

- The current $I_1 = V/R = 32/2.18 = \mathbf{14.67\ A}$
- Power dissipated in $4\ \Omega$ resistor is
 $P = V^2/R_3 = 32^2/4 = \mathbf{256\ W}$
- The current $I_2 = I_1 = \mathbf{14.67\ A}$