
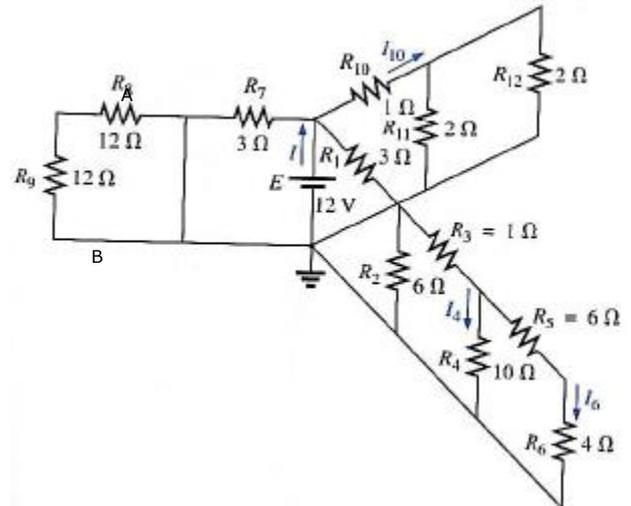


**Q** - For the multiple ladder configuration of Figure,

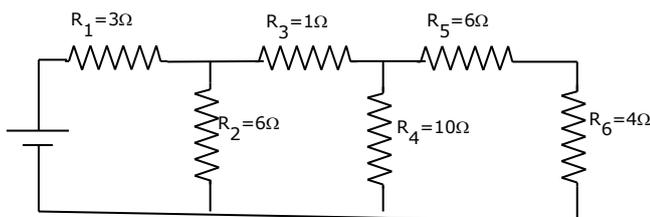- Determine current  $I$  through battery
- Calculate current  $I_4$  through resistance  $R_4$
- Find current  $I_6$  through resistance  $R_6$
- Find current  $I_{10}$  through resistance  $R_{10}$



The three ladders are parallel to each other and hence can be treated separately. For the first ladder



$R_5$  and  $R_6$  are in series and their equivalent is  $6 + 4 = 10 \Omega$

This is in parallel with  $R_4$  and makes a total  $10 \cdot 10 / (10 + 10) = 5 \Omega$

This is in series with  $R_3$  and hence the total is  $5 + 1 = 6 \Omega$

This resistance is in parallel with  $R_2$  makes it  $6 \cdot 6 / (6 + 6) = 3 \Omega$

And this is in series with  $R_1$  makes total resistance of the ladder equal to  $6 \Omega$

Total current through the first ladder is  $I_1 = 12/6 = 2 \text{ A}$

Now for the second ladder

The ends of the series of  $R_8$  and  $R_9$  are connected by a conducting wire and hence the net resistance will be zero. The only effective resistor is  $R_7$  and hence the current in this ladder will be

$$I_7 = 12/3 = 4 \text{ A}$$

For the third ladder

In the third ladder  $R_{11}$  and  $R_{12}$  each of  $2 \Omega$  are in parallel equals to  $1 \Omega$  and in series with  $R_{10}$  makes total resistance of the ladder equal to  $2 \Omega$ . Hence the current in the third ladder will be

$$I_{10} = 12/2 = 6 \text{ A}$$

a. The current  $I$  through the battery is the total current given to the three ladder and will be equal to

$$I = I_1 + I_7 + I_{10} = 2 + 4 + 6 = \mathbf{12 \text{ A}}$$

b.c. As the equivalent of  $R_3$ ,  $R_4$ ,  $R_5$  and  $R_6$  is  $6 \Omega$  which is in parallel with  $R_2 = 6 \Omega$ . The current will equally divided in the two branches and hence current through  $R_3$  is  $1 \text{ A}$  which is again equally divided in to the series of  $R_5$  and  $R_6$  and  $R_4$  in parallel hence

$$I_4 = I_6 = \mathbf{0.5 \text{ A}}$$

d.

$I_{10}$  is the total current through the third ladder and equal to  $\mathbf{6 \text{ A}}$  as shown above.