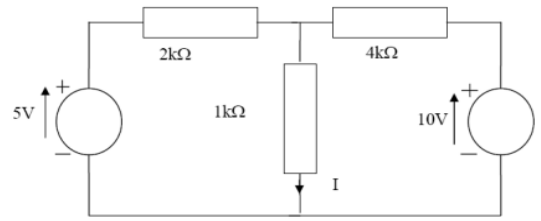


Q- Consider the circuit in fig below with two ideal voltage sources. Calculate the current  $I$  in the  $1\text{ k}\Omega$  resistor using the superposition theorem.



The superposition theorem states that "total current in any part of a linear circuit equals the algebraic sum of the currents produced by each source separately"

If the battery of  $10\text{ V}$  is short circuited then the parallel combination of  $1\text{K}\Omega$  and  $4\text{ K}\Omega$  is in series with  $2\text{ K}\Omega$  resistance and hence equivalent resistance of the circuit will be

$$R = 2 + \frac{4 \cdot 1}{4 + 1} = 2.8\text{ K}\Omega$$

The current in the circuit will be

$$I = 5 / 2.8\text{K} = 1.786\text{ mA}$$

This current will be distributed in the resistances of  $1\text{K}\Omega$  and  $4\text{ k}\Omega$  in the ratio of  $4:1$  and hence the current in  $1\text{ K}\Omega$  resistor will be

$$I_1 = 1.786 (4/5) = 1.428\text{ mA}$$

Now if the battery of  $5\text{ V}$  is short circuited then the parallel combination of  $1\text{K}\Omega$  and  $2\text{ K}\Omega$  is in series with  $4\text{ K}\Omega$  resistance and hence equivalent resistance of the circuit will be

$$R' = 4 + \frac{2 \cdot 1}{2 + 1} = 4.67\text{ K}\Omega$$

The current in the circuit will be

$$I' = 10 / 4.667\text{K} = 2.143\text{ mA}$$

This current will be distributed in the resistances of  $1\text{K}\Omega$  and  $2\text{ k}\Omega$  in the ratio of  $2:1$  and hence the current in  $1\text{ K}\Omega$  resistor will be

$$I_2 = 2.143 (2/3) = 1.428\text{ mA}$$

Hence the total current in  $1\text{K}\Omega$  resistance will be

$$I = I_1 + I_2 = 1.428 + 1.428 = 2.856\text{ mA}$$

(can be done easily using Kirchoff's law)