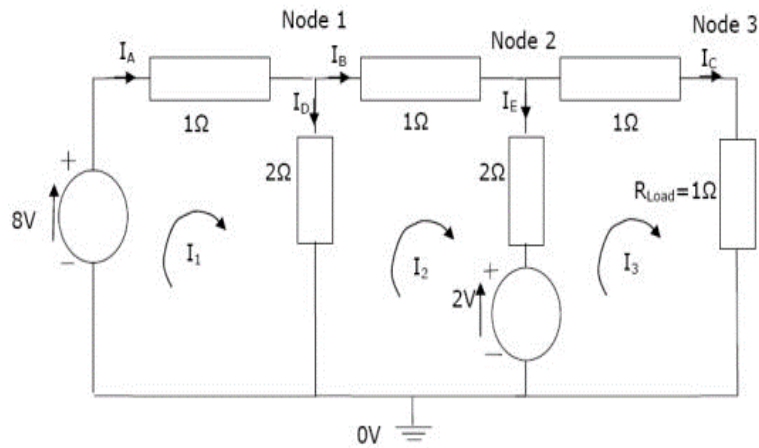


Q- Two ideal constant voltage sources and six resistors are connected in a circuit as shown. The right most resistor is the load. Using mesh analysis calculate currents I_1 , I_2 and I_3 .

- i) In a closed loop (mesh) the net potential drop will be zero.
- ii) Due to a battery the potential is gained, hence potential drop is taken negative
- iii) The potential drop across a resistance is given by $R \cdot I$



Now writing mesh equations for the three loops respectively we get

For the first loop

$$-8 + 1 \cdot I_1 + 2 \cdot (I_1 - I_2) = 0$$

$$\text{Or } 3 I_1 - 2 I_2 = 8 \quad \text{----- (1)}$$

For second loop

$$-2 \cdot (I_1 - I_2) + 1 \cdot I_2 + 2 \cdot (I_2 - I_3) + 2 = 0$$

$$\text{Or } 2 I_1 - 5 I_2 + 2 I_3 = 2 \quad \text{----- (2)}$$

For third loop

$$-2 \cdot (I_2 - I_3) + 1 \cdot I_3 + 1 \cdot I_3 - 2 = 0$$

$$\text{Or } -2 I_2 + 4 I_3 = 2 \quad \text{----- (3)}$$

Solving the three equations we get

$$I_1 = 3.75 \text{ A}; \quad I_2 = 1.625 \text{ A}; \quad I_3 = 1.312 \text{ A}$$